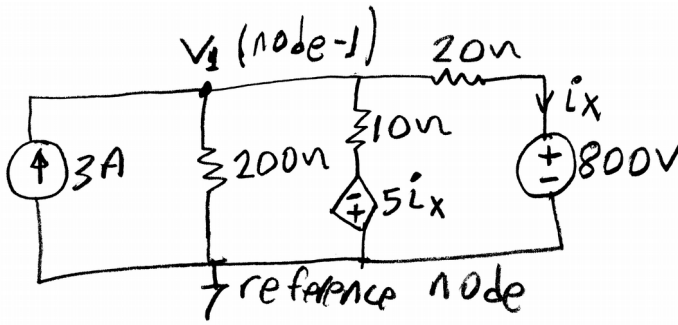


Student Name:

Student No :

Daytime: ☐ Evening: ☐1-(50) Use the node-voltage method to find V_1 in the circuit shown below2-a)(50) Find the mesh currents i_1, i_2 , and i_3 in the circuit shown below.b)(10) Find V_1 .