


CHAPTER-4

Techniques of Circuit Analysis

Structure




- Terminology
- Node--Voltage Method
- Mesh--Current Method
- Source Transformation
- Thévenin and Norton Equivalents
- Maximum Power Transfer
- Superpositon

Circuit with Realistic Resistors

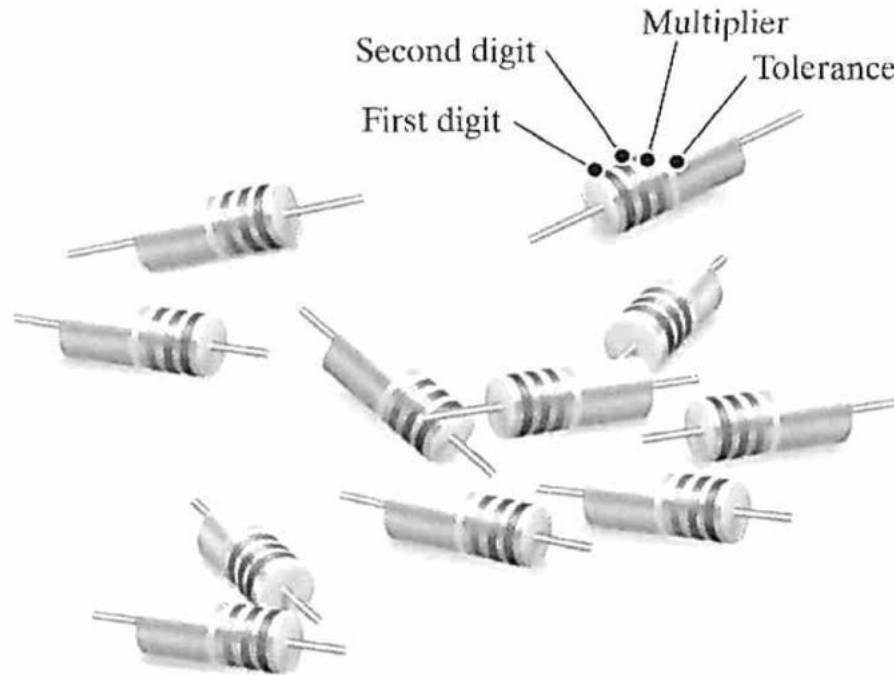

Terminology

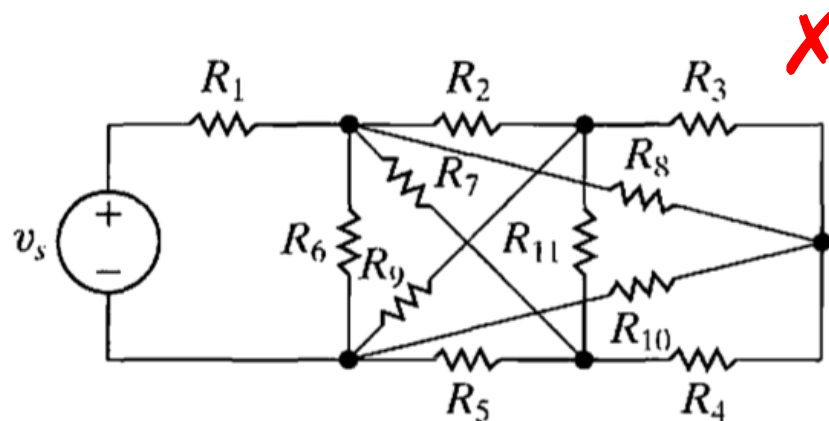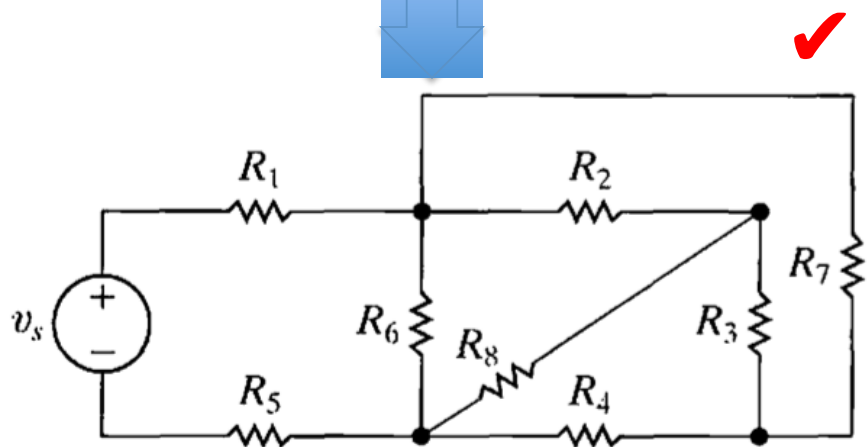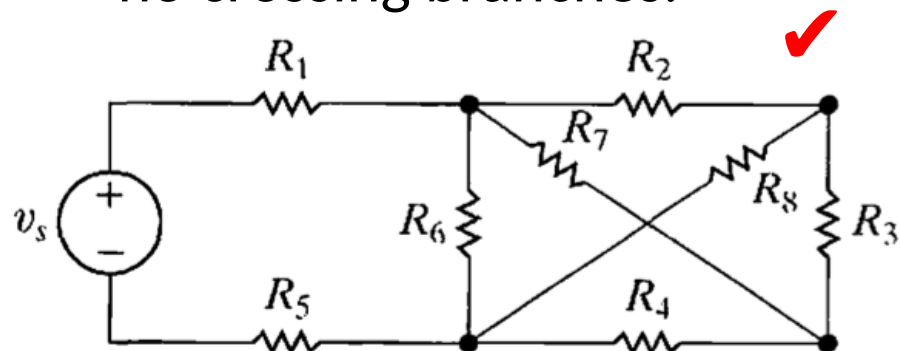Planar circuits: the circuits that can be drawn on a plane with no crossing branches.




More Terms for Describing Circuits

Name	Definition
node	A point where two or more circuit elements join
essential node	A node where three or more circuit elements join
path	A trace of adjoining basic elements with no elements included more than once
branch	A path that connects two nodes
essential branch	A path which connects two essential nodes without passing through an essential node
loop	A path whose last node is the same as the starting node
mesh	A loop that does not enclose any other loops
planar circuit	A circuit that can be drawn on a plane with no crossing branches


Example #1

For the circuit in Fig. 4.3, identify:

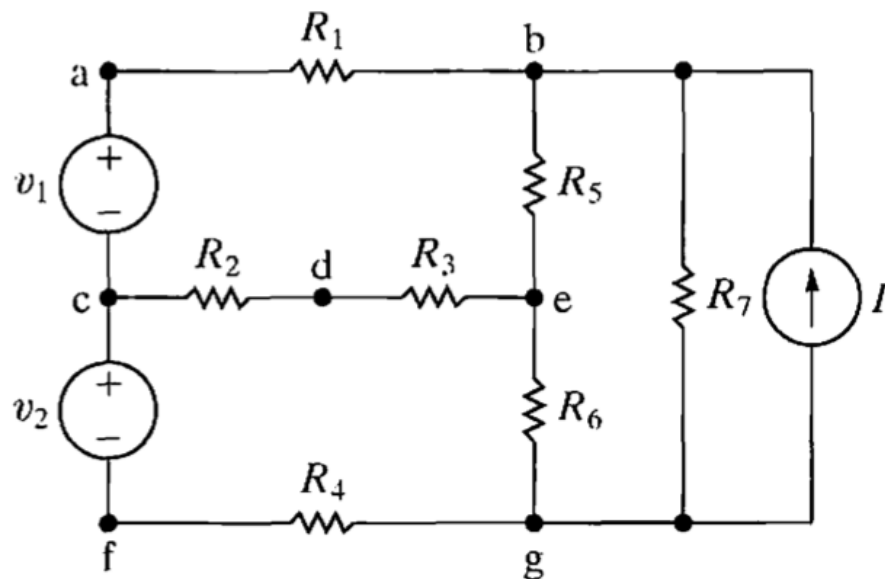- a) all nodes.
- b) all essential nodes.
- c) all branches.
- d) all essential branches.
- e) all meshes.
- f) two paths that are not loops or essential branches.
- g) two loops that are not meshes.



Solution for Example #1

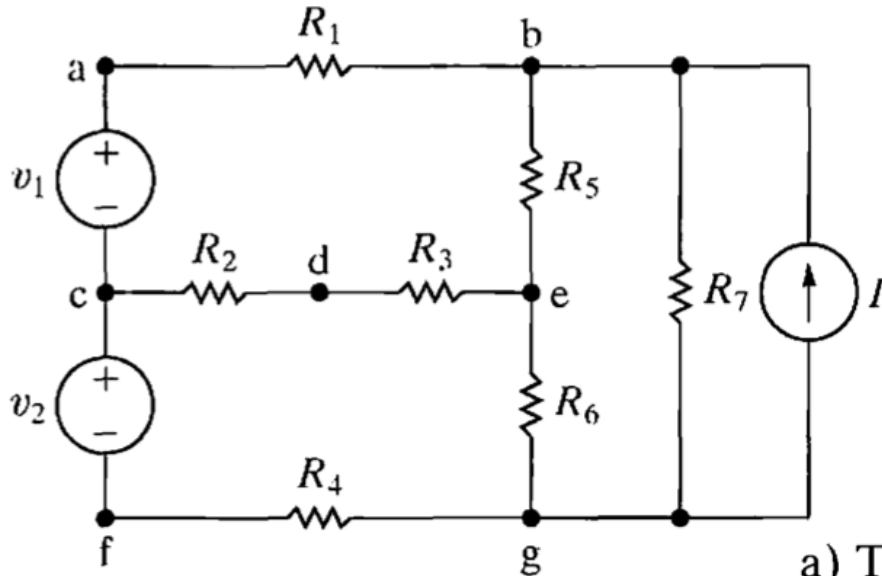

- The nodes are a, b, c, d, e, f, and g.
- The essential nodes are b, c, e, and g.
- The branches are v_1 , v_2 , R_1 , R_2 , R_3 , R_4 , R_5 , R_6 , R_7 , and I .
- The essential branches are $v_1 - R_1$, $R_2 - R_3$, $v_2 - R_4$, R_5 , R_6 , R_7 , and I .
- The meshes are $v_1 - R_1 - R_5 - R_3 - R_2$, $v_2 - R_2 - R_3 - R_6 - R_4$, $R_5 - R_7 - R_6$, and $R_7 - I$.

Simultaneous Equatons

b : number of branches; n : number of nodes

Kirchhoff's current law: $n-1$ independent equations

Kirchhoff's voltage law: $b-(n-1)$ independent equations


b_e : number of essential branches

n_e : number of essential nodes

Kirchhoff's current law: n_e-1 independent equations

Kirchhoff's voltage law: $b_e-(n_e-1)$ independent equations

Example #2

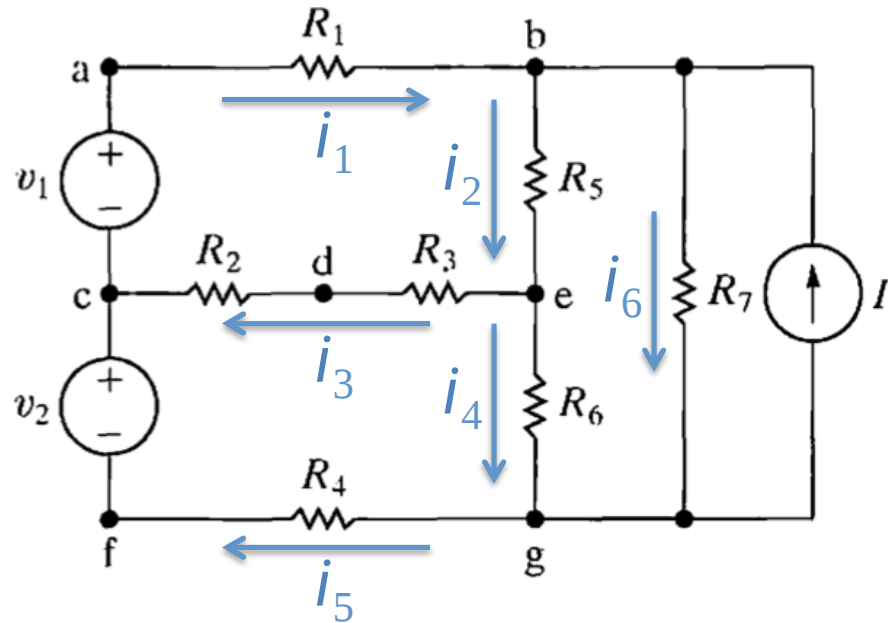

Seven essential branches

Four essential nodes:

$$-i_1 + i_2 + i_6 - I = 0,$$

$$i_1 - i_3 - i_5 = 0,$$

$$i_3 + i_4 - i_2 = 0.$$


Three meshes:

$$R_1 i_1 + R_5 i_2 + i_3 (R_2 + R_3) - v_1 = 0,$$

$$-i_3 (R_2 + R_3) + i_4 R_6 + i_5 R_4 - v_2 = 0,$$

$$-i_2 R_5 + i_6 R_7 - i_4 R_6 = 0.$$

Node-Voltage Method

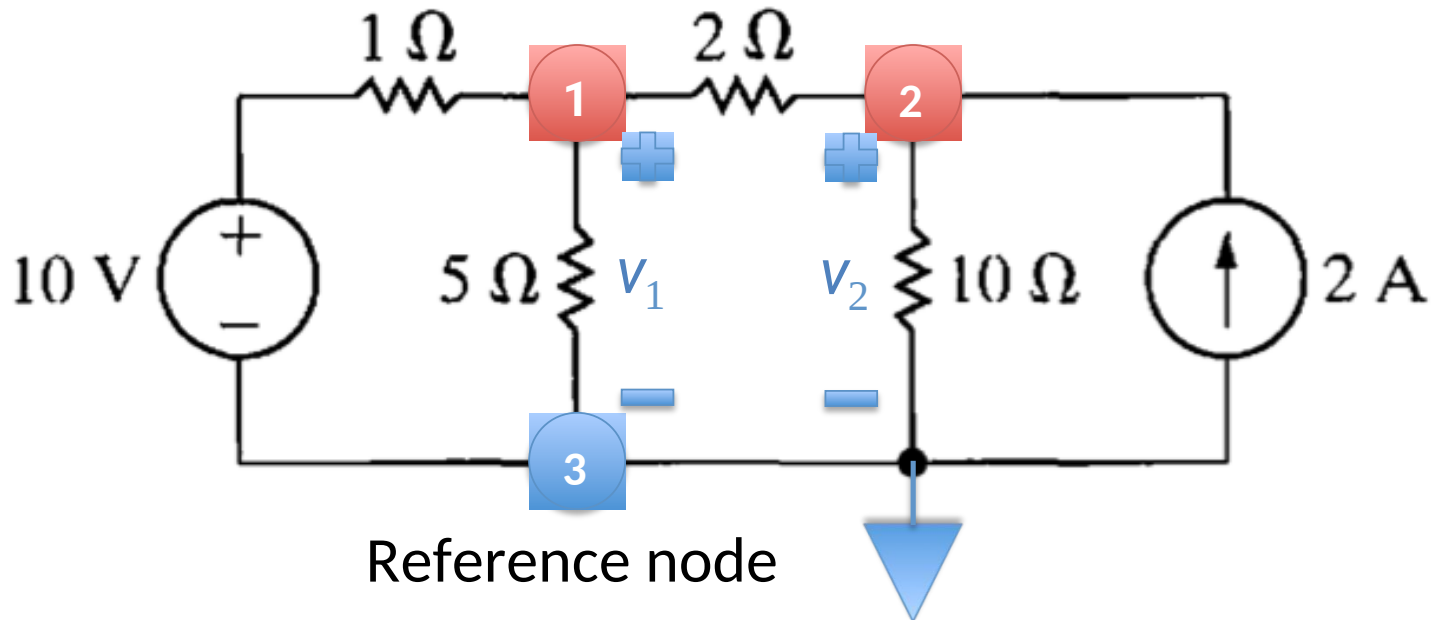


$$\text{Node 1: } \frac{v_1 - 10}{1} + \frac{v_1}{5} + \frac{v_1 - v_2}{2} = 0$$

$$\text{Node 2: } \frac{v_2 - v_1}{2} + \frac{v_2}{10} - 2 = 0$$

Dependent Sources

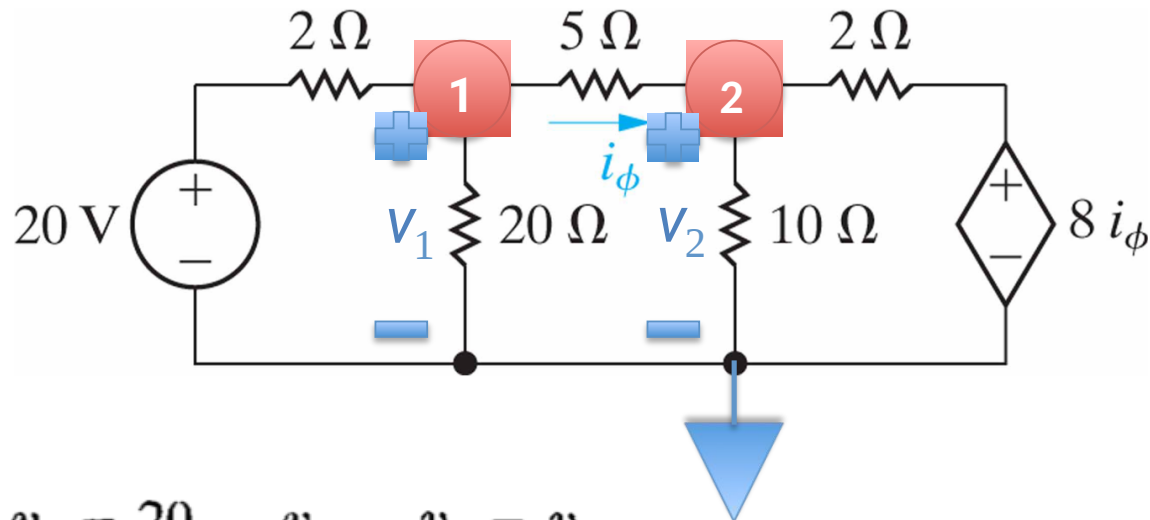Use the node-voltage method to find the power dissipated in the 5Ω resistor in the circuit.




$$\text{Node 1: } \frac{v_1 - 20}{2} + \frac{v_1}{20} + \frac{v_1 - v_2}{5} = 0$$

$$\text{Node 2: } \frac{v_2 - v_1}{5} + \frac{v_2}{10} + \frac{v_2 - 8i_\phi}{2} = 0$$


$$i_\phi = \frac{v_1 - v_2}{5}$$

Special Case

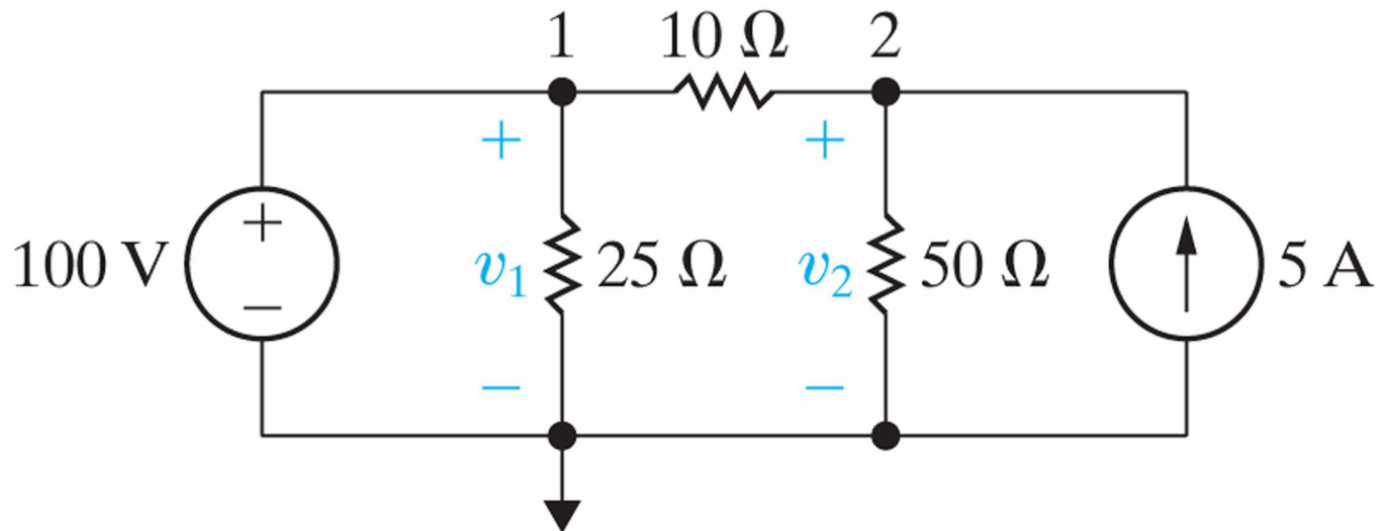


$$\frac{v_2 - v_1}{10} + \frac{v_2}{50} - 5 = 0$$

$$\underline{v_1 = 100 \text{ V}}$$

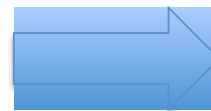


$$v_2 = 125 \text{ V}$$

Supernode

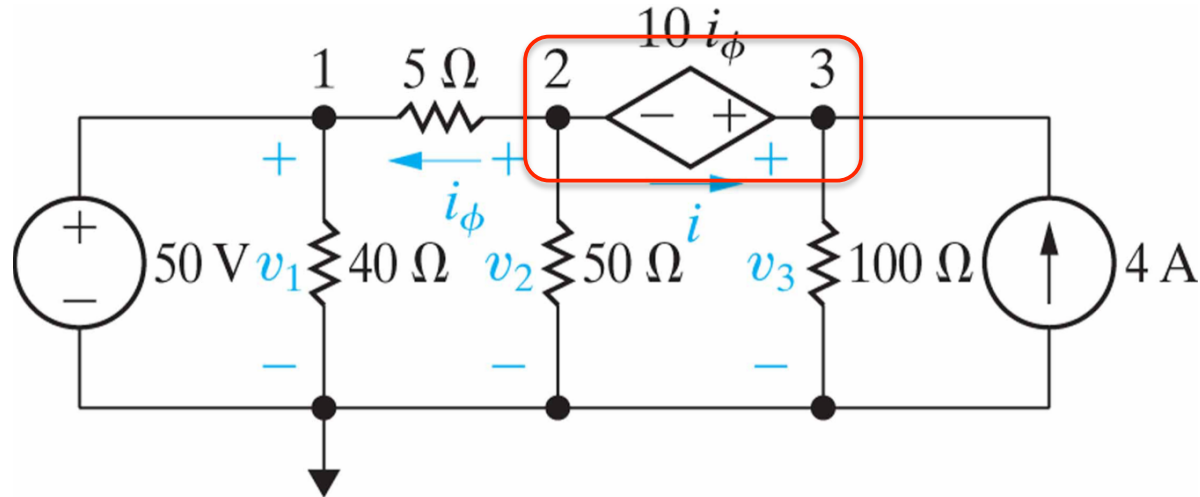

$$\text{Node 2: } \frac{v_2 - v_1}{5} + \frac{v_2}{50} + i = 0$$
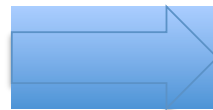
$$\text{Node 3: } \frac{v_3}{100} - i - 4 = 0$$




$$\frac{v_2 - v_1}{5} + \frac{v_2}{50} + \frac{v_3}{100} - 4 = 0$$

$$i_\phi = \frac{v_2 - 50}{5}$$

$$v_3 = v_2 + 10i_\phi$$

Example #3

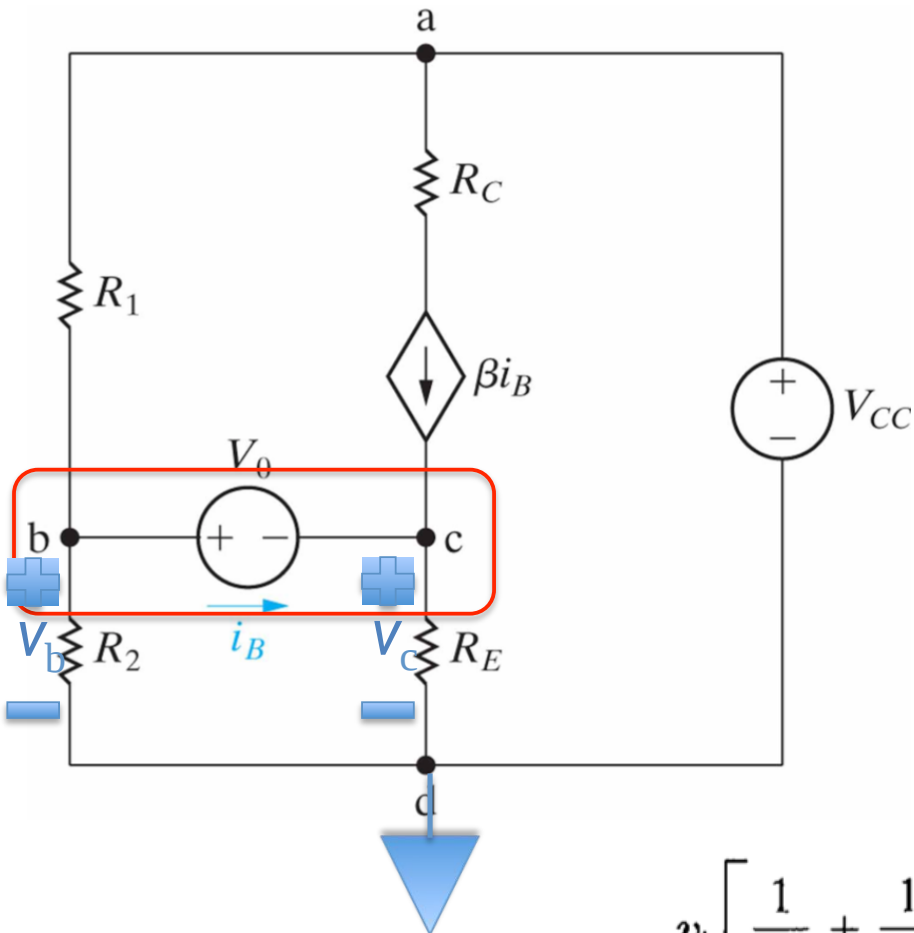

The circuit has four essential nodes: Nodes **a** and **d** are connected by an independent voltage source as are nodes **b** and **c**. Therefore the problem reduces to finding a single unknown node voltage, because $(n - 1) - 2 = 1$


$$\frac{v_b}{R_2} + \frac{v_b - V_{CC}}{R_1} + \frac{v_c}{R_E} - \beta i_B = 0$$

$$v_c = (i_B + \beta i_B) R_E$$

$$v_c = v_b - V_0$$

$$v_b \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{(1 + \beta) R_E} \right] = \frac{V_{CC}}{R_1} + \frac{V_0}{(1 + \beta) R_E}$$


Mesh-Current Method

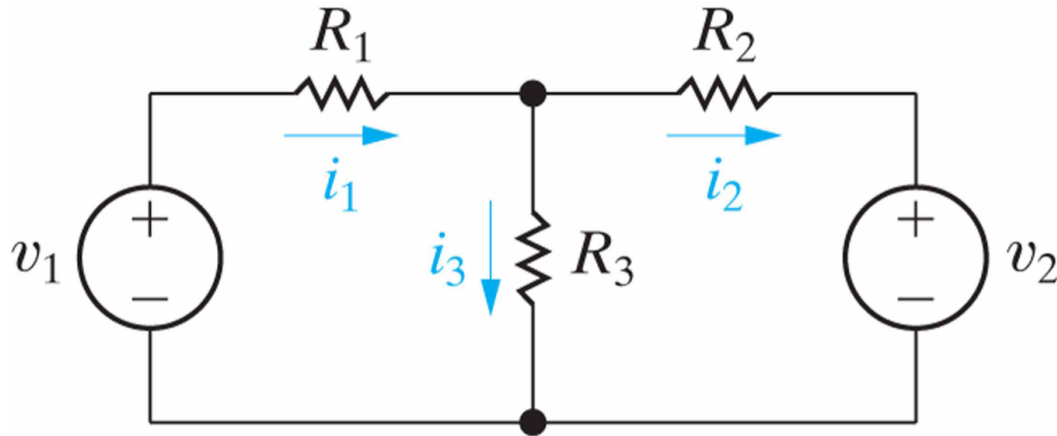


$$b_e=3 \quad n_e=2 \quad b_e-(n_e-1)=2$$

$$v_1 = i_a R_1 + (i_a - i_b) R_3$$

$$-v_2 = (i_b - i_a) R_3 + i_b R_2$$

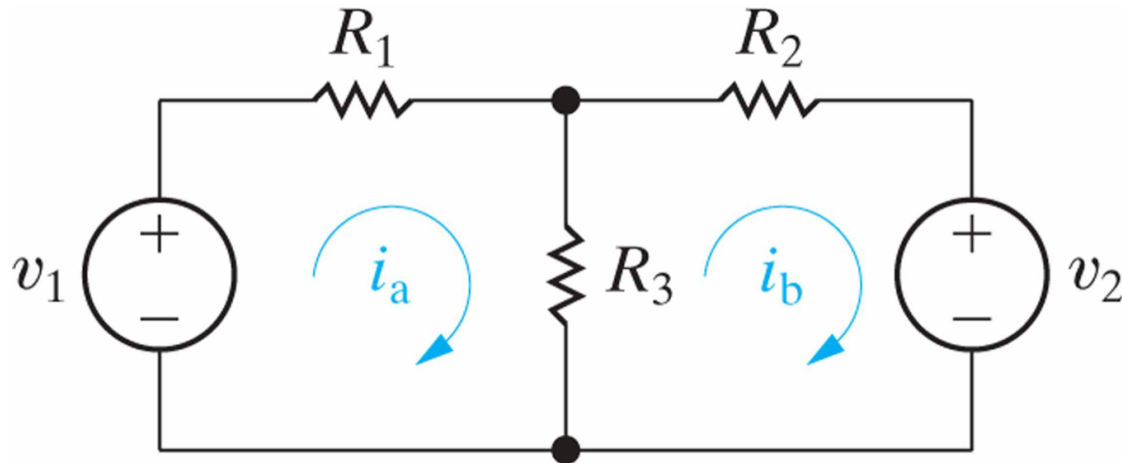

Dependent Sources

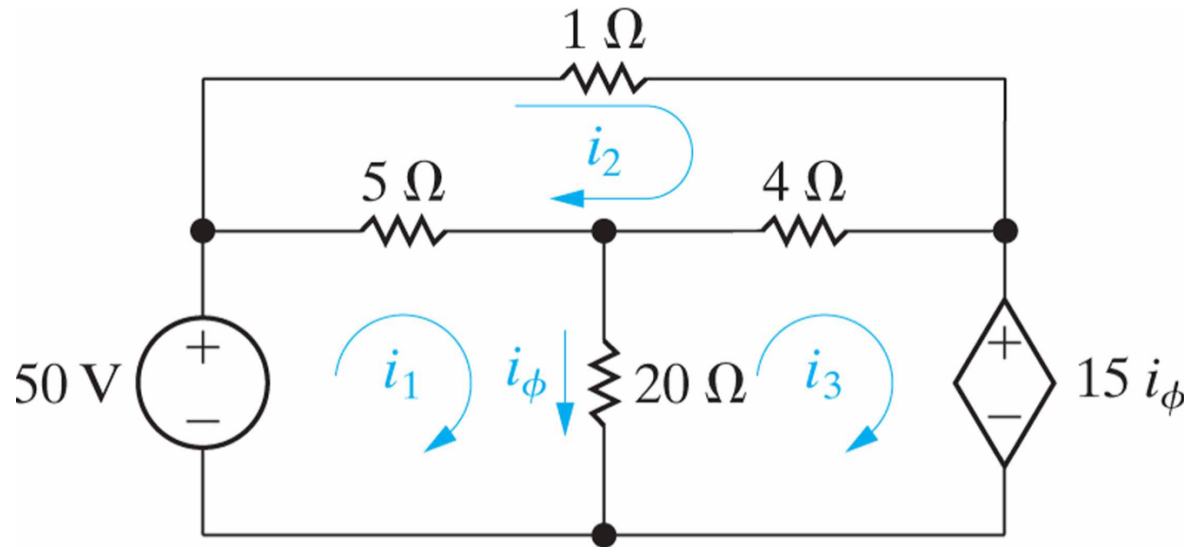


Mesh 1: $50 = 5(i_1 - i_2) + 20(i_1 - i_3)$

Mesh 2: $0 = 5(i_2 - i_1) + 1i_2 + 4(i_2 - i_3)$

Mesh 3: $0 = 20(i_3 - i_1) + 4(i_3 - i_2) + 15i_\phi$


Constraint: $i_\phi = i_1 - i_3$

Special Case

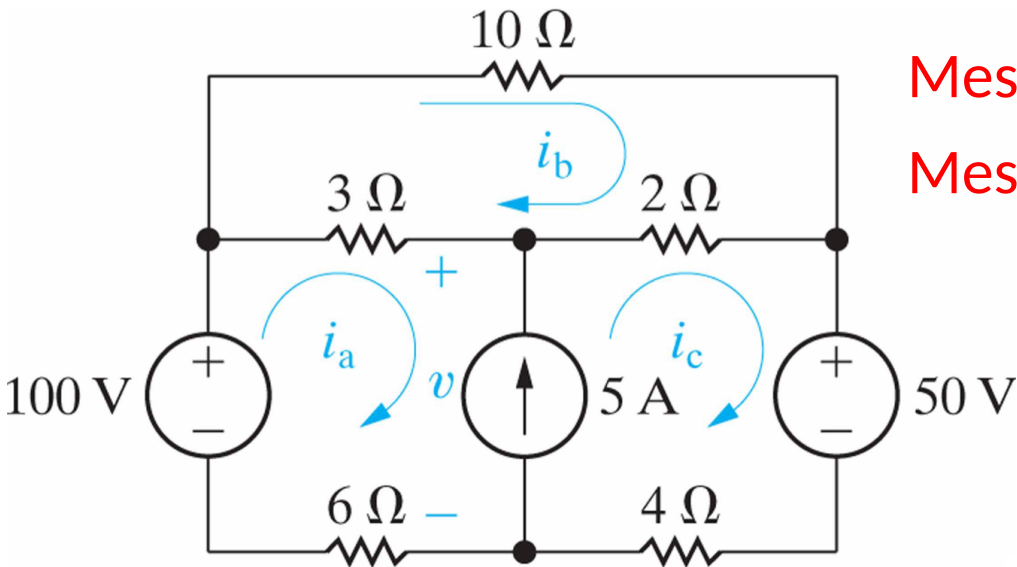


Mesh a: $100 = 3(i_a - i_b) + v + 6i_a$

Mesh c: $-50 = 4i_c - v + 2(i_c - i_b)$

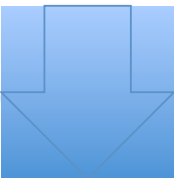

 $50 = 9i_a - 5i_b + 6i_c$

Mesh b: $0 = 3(i_b - i_a) + 10i_b + 2(i_b - i_c)$

Constraint: $i_c - i_a = 5$

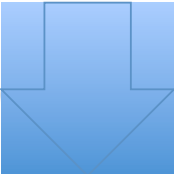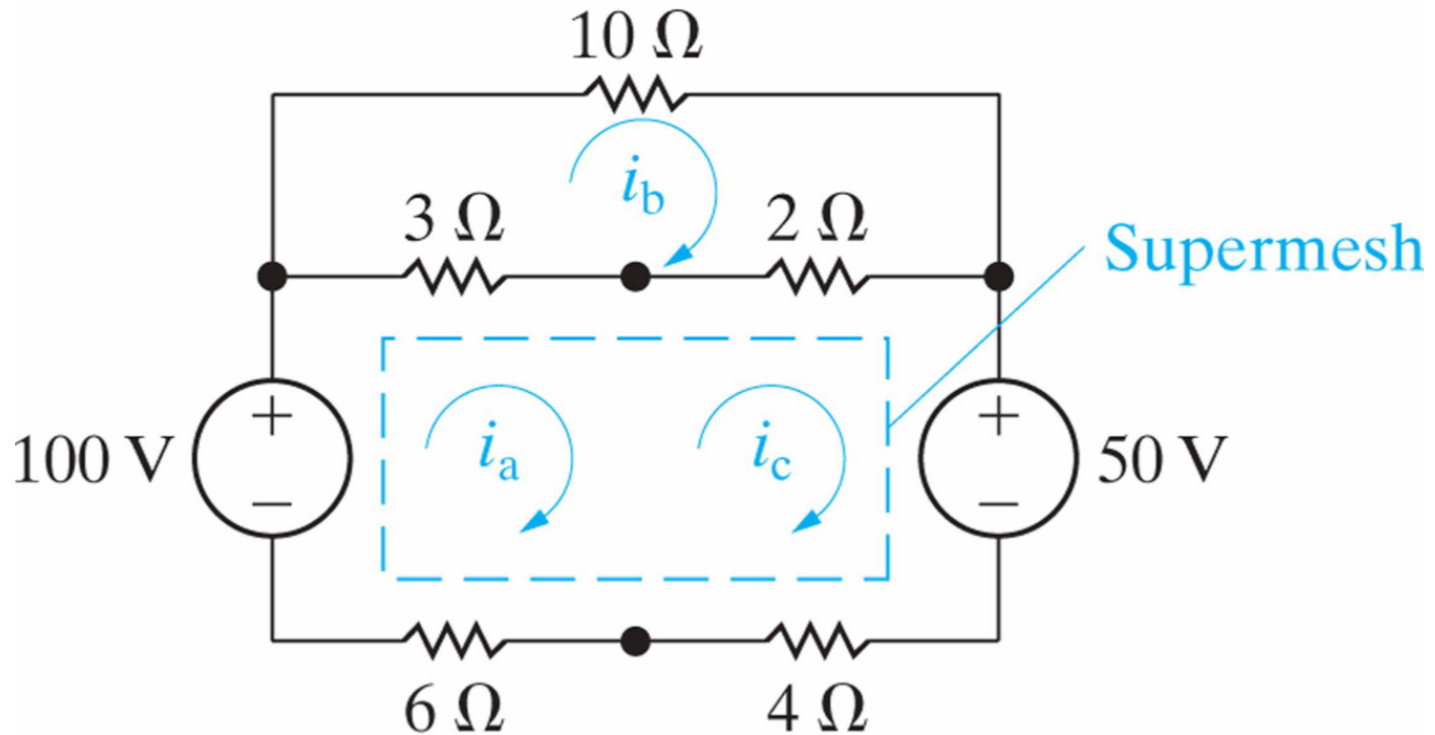
 $i_a = 1.75 \text{ A}, \quad i_b = 1.25 \text{ A}, \quad \text{and} \quad i_c = 6.75 \text{ A}$

Supermesh



$$-100 + 3(i_a - i_b) + 2(i_c - i_b) + 50 + 4i_c + 6i_a = 0$$




$$50 = 9i_a - 5i_b + 6i_c$$


Node-Voltage vs. Mesh-Current

- Does one of the methods result in **fewer simultaneous equations** to solve?
- Does the circuit **contain supernodes**? If so, using the node-voltage method will permit you to reduce the number of equations to be solved.
- Does the circuit **contain supermeshes**? If so, using the mesh-current method will permit you to reduce the number of equations to be solved.
- Will solving some portion of the circuit give the requested solution? If so, which method is most efficient for solving just the pertinent portion of the circuit?

Source Transformations

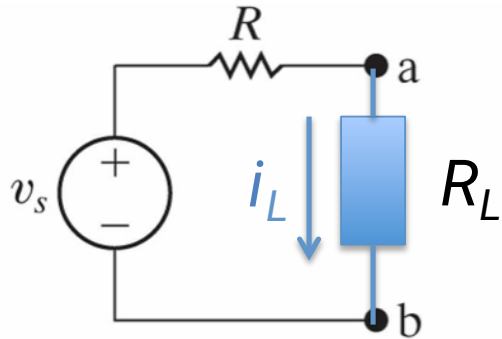


(a)

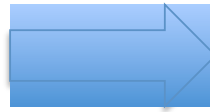


$$i_L = \frac{v_s}{R + R_L}$$



$$i_s = \frac{v_s}{R}$$

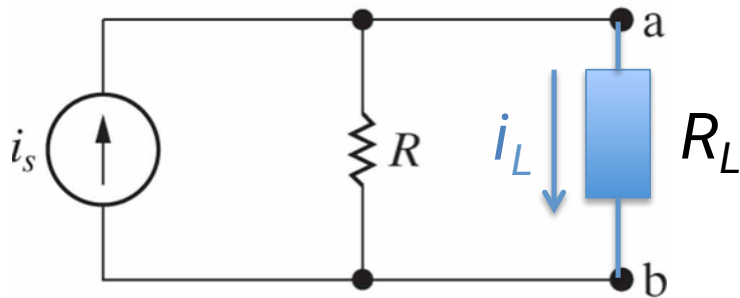

(b)

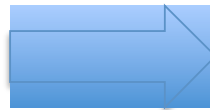

$$i_L = \frac{R}{R + R_L} i_s$$

Equivalent circuits with respect to terminals a and b


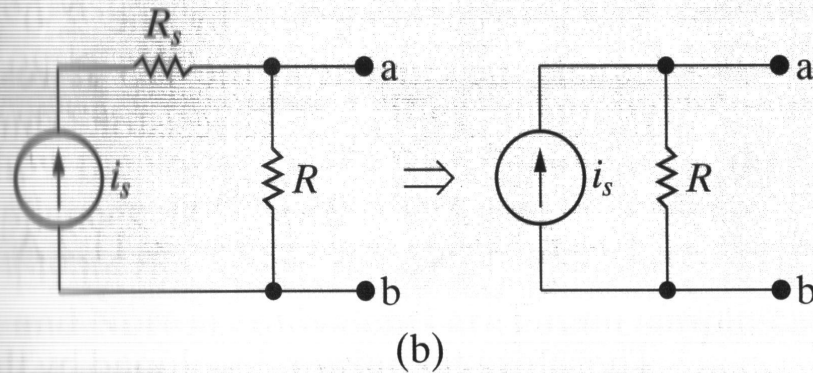
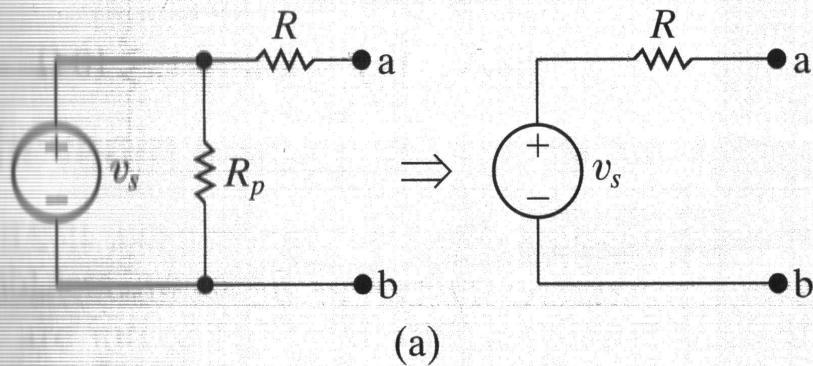






Figure 4.39 Equivalent circuits containing a resistance in parallel with a voltage source or in series with a current source.

Example #4

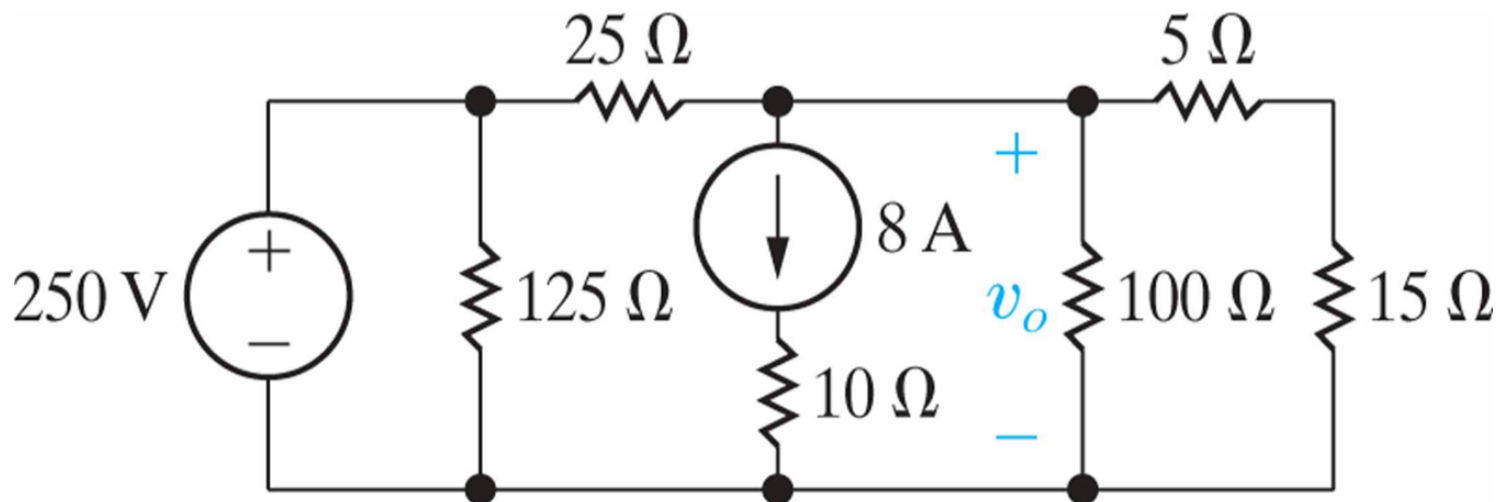- (a) Use source transformations to find the voltage v_o in the circuit.
- (b) Find the power developed by the 250 V voltage source.
- (c) Find the power developed by the 8 A current source.



Solution for Example #4

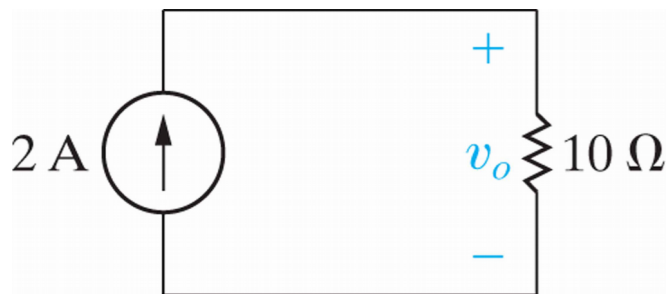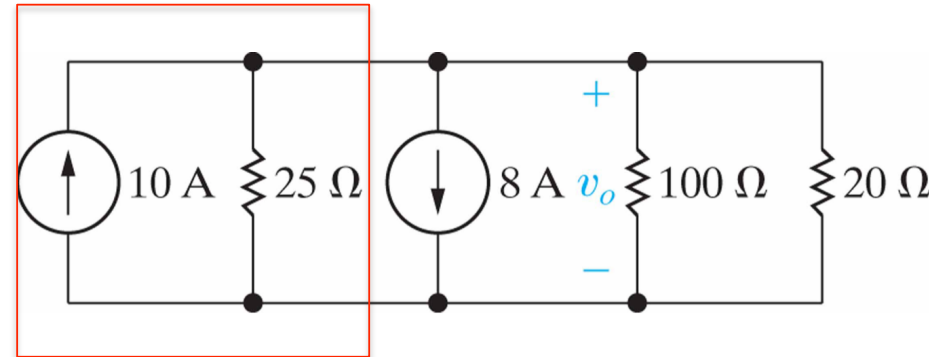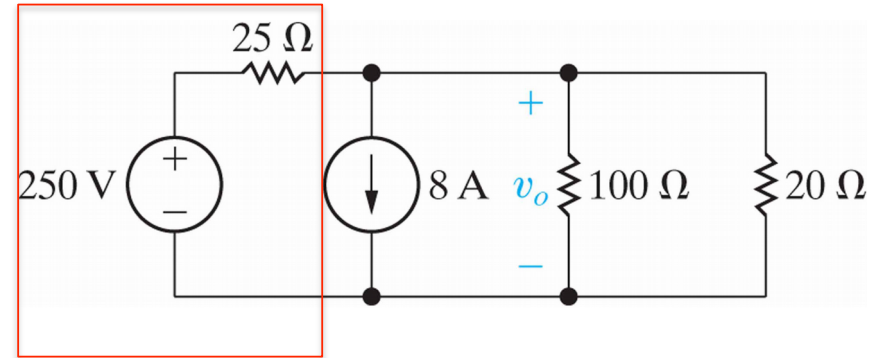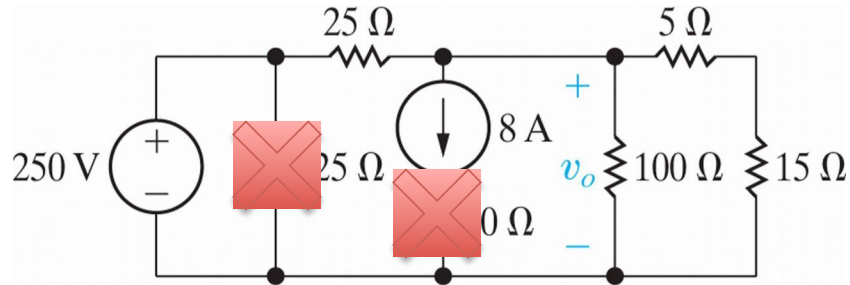

Thévenin and Norton Equivalents


- **Thévenin and Norton equivalents** are circuit simplification techniques that **focus on terminal behavior** and thus are extremely valuable aids in analysis.
- **Thevenin equivalent circuit:** an independent voltage source V_{Th} in series with a resistor R_{Th} , which replaces an interconnection of sources and resistors.
- **Norton equivalent circuit:** consists of an independent current source in parallel with the Norton equivalent resistance,

Thévenin Equivalent

A resistive network containing independent and dependent sources

• a
• b

(a)


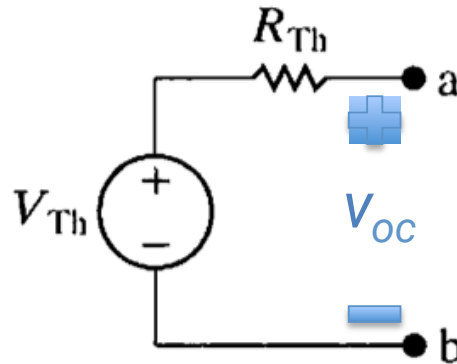


(b)



$$V_{Th} = V_{oc}$$

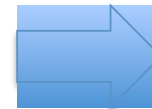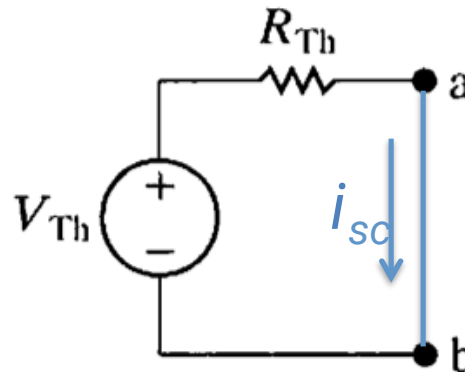
Thévenin voltage V_{Th} equals to the open-circuit voltage in the original circuit.



$$R_{Th} = V_{Th}/i_{sc} = V_{oc}/i_{sc}$$


Thévenin resistance R_{Th} is the ratio of the open-circuit voltage to the short-circuit current.

Example #5

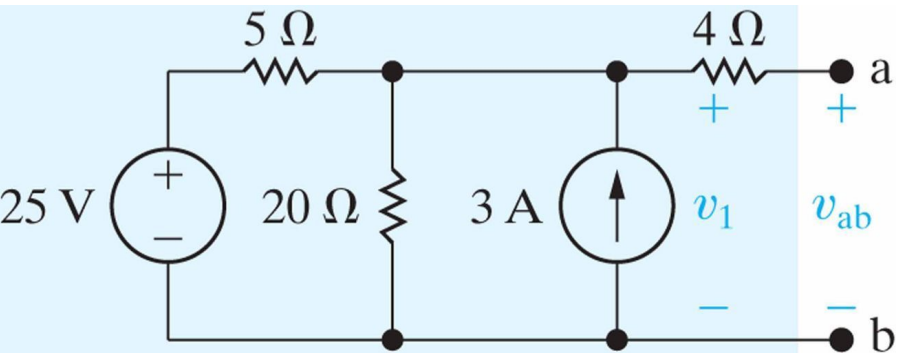

$$\frac{v_1 - 25}{5} + \frac{v_1}{20} - 3 = 0$$


$$V_{Th} = v_1 = 32 \text{ V}$$

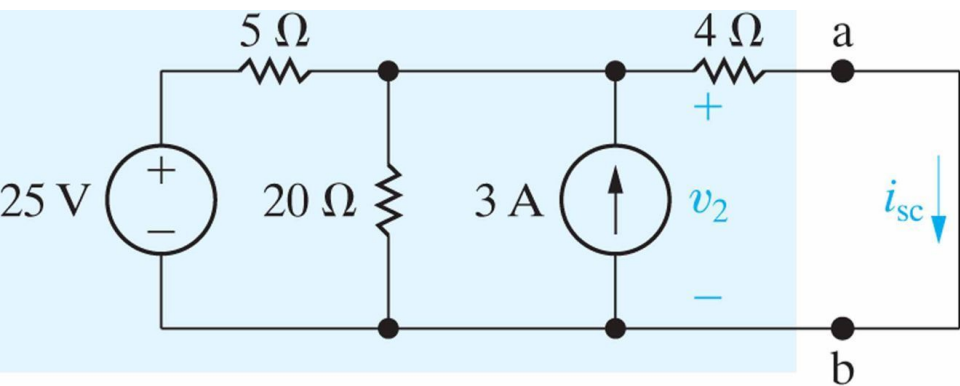

$$\frac{v_2 - 25}{5} + \frac{v_2}{20} - 3 + \frac{v_2}{4} = 0$$


$$v_2 = 16 \text{ V} \quad i_{sc} = \frac{16}{4} = 4 \text{ A}$$
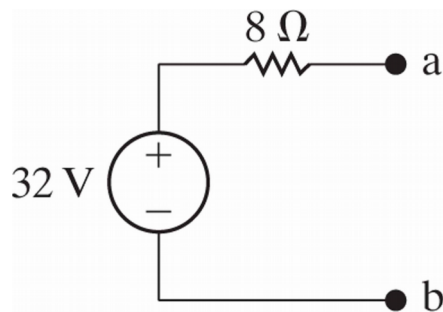
$$R_{Th} = V_{Th} / i_{sc} = 8 \text{ A}$$




Thévenin Equivalents


Norton Equivalent

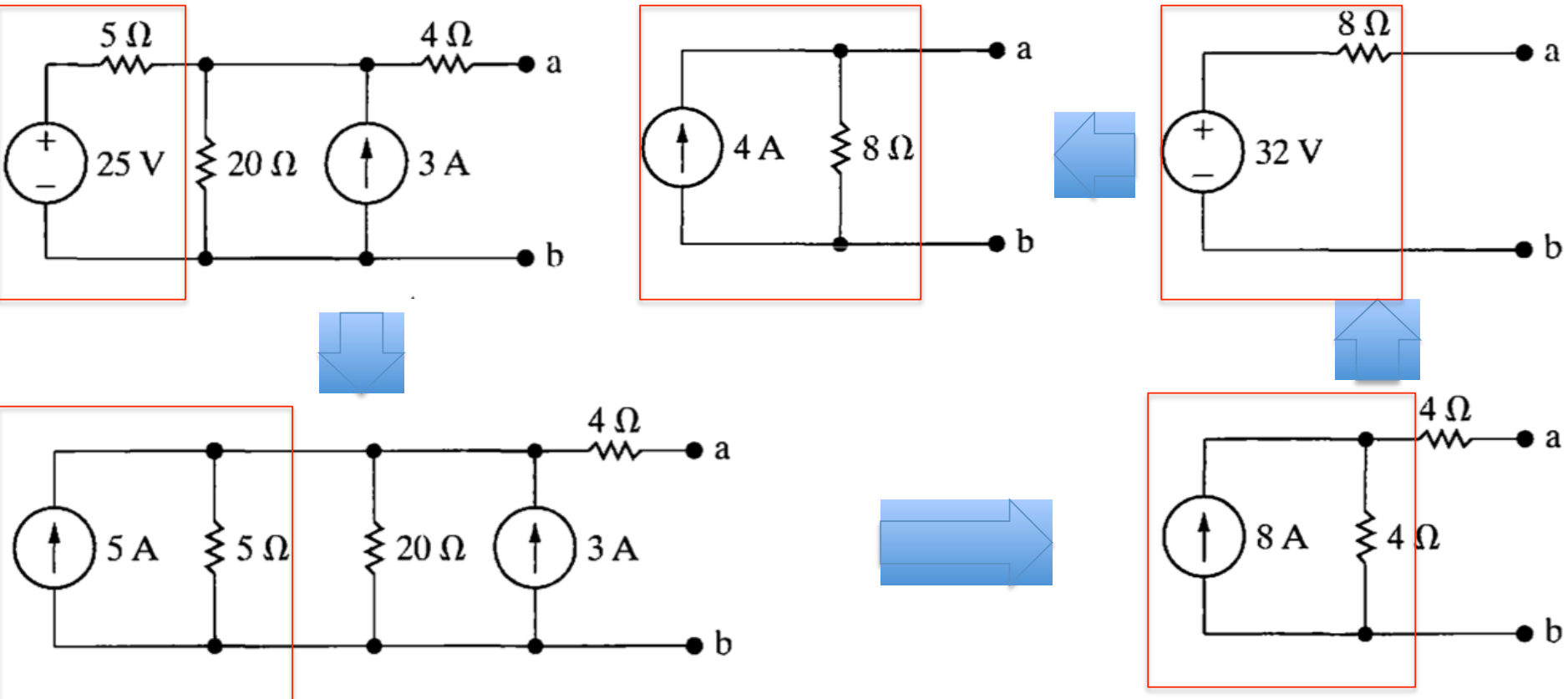

More on Thevenin Equivalent

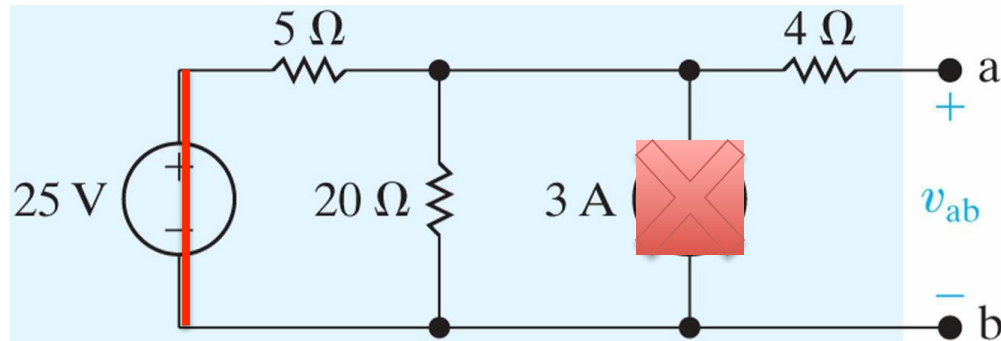

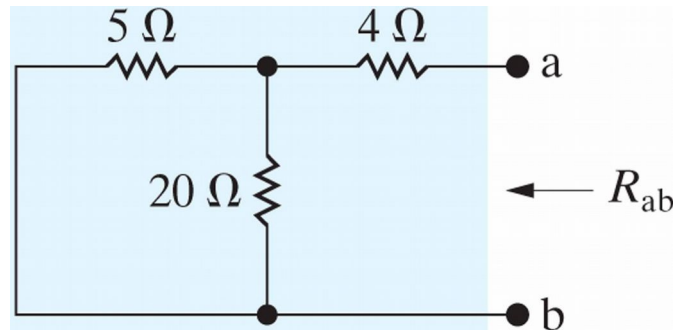A **voltage source** is deactivated by replacing it with a **short circuit**.
A **current source** is deactivated by replacing it with an **open circuit**.






$$R_{ab} = R_{Th} = 4 + \frac{5 \times 20}{25} = 8 \, \Omega$$

Maximum Power Transfer

Power Transfer

- I⌘ The first emphasizes the **efficiency** of the power transfer.
 - u⌘ **Power utility systems** are a good example of this type because they are concerned with the generation, transmission, and distribution of large quantities of electric power.
- I⌘ The second basic type of system emphasizes **the amount of power** transferred. ✓
 - I⌘ **Communication and instrumentation systems** are good examples because in the transmission of information, or data, via electric signals, the power available at the transmitter or detector is limited

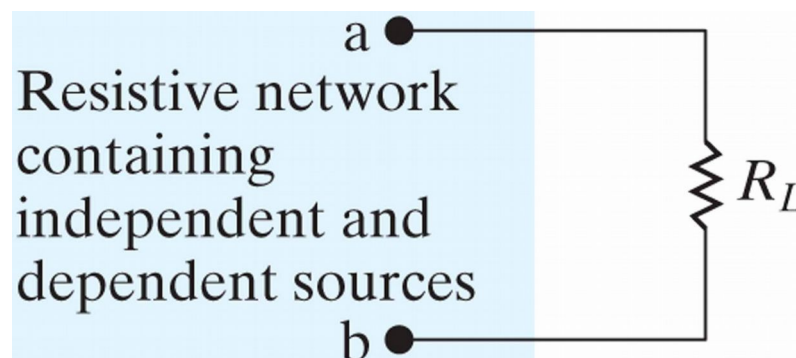

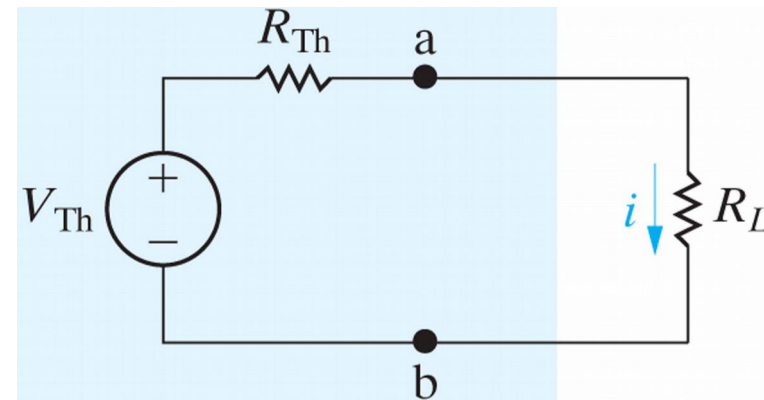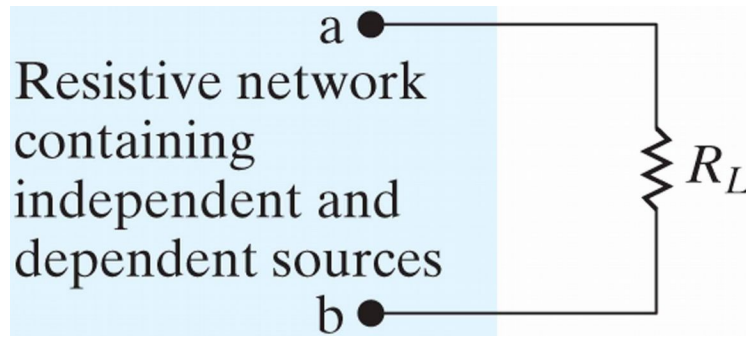

$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

$$\frac{dp}{dR_L} = V_{Th}^2 \left[\frac{(R_{Th} + R_L)^2 - R_L \cdot 2(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right]$$

p is maximized when the derivative is zero, thus we have

$$(R_{Th} + R_L)^2 = 2R_L(R_{Th} + R_L)$$



$$R_L = R_{Th} \quad p_{\max} = \frac{V_{Th}^2 R_L}{(2R_L)^2} = \frac{V_{Th}^2}{4R_L}$$

Summary

- Basic terms: node, essential node, path, branch, essential branch, mesh, and planar circuit.
- Node-voltage and mesh-current methods
- Source transformations
- Thévenin and Norton equivalents
- Maximum power transfer
-