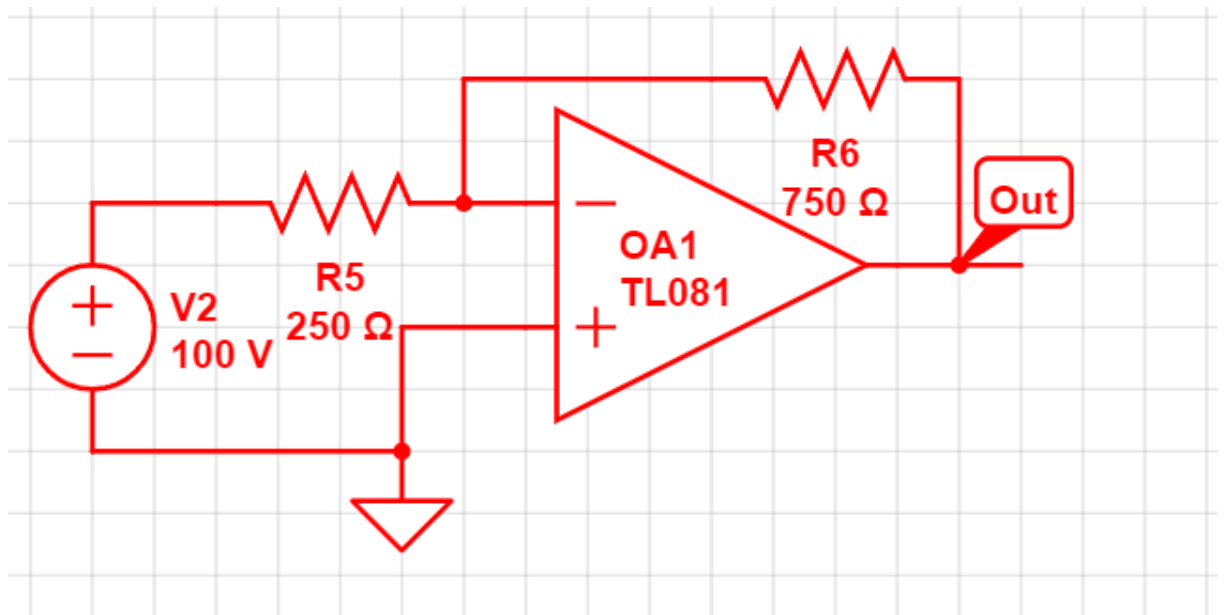


1) What is short circuit?

2) What is the voltage on Out node for given ideal opamp?



3) The opamp goes into saturation at the voltage level 9V. Find the voltage on R3

