


Adı Soyadı:
Numarası:

Circuit Laboratory Final


Student must send the answers fkumru@cu.edu.tr mail address. Mail Subject: Write your name, surname, and nummber. If you do not write , your answer can be rejected.

All questions can be send by photo.

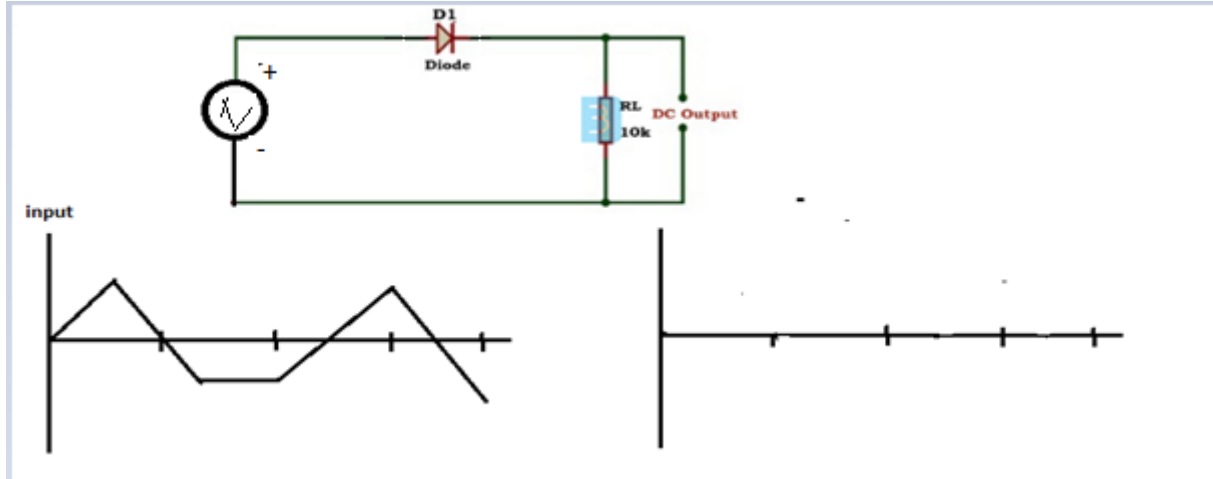Q1)For given circuit and input voltage, draw the output response of circuit . (You can use another paper to draw answer)



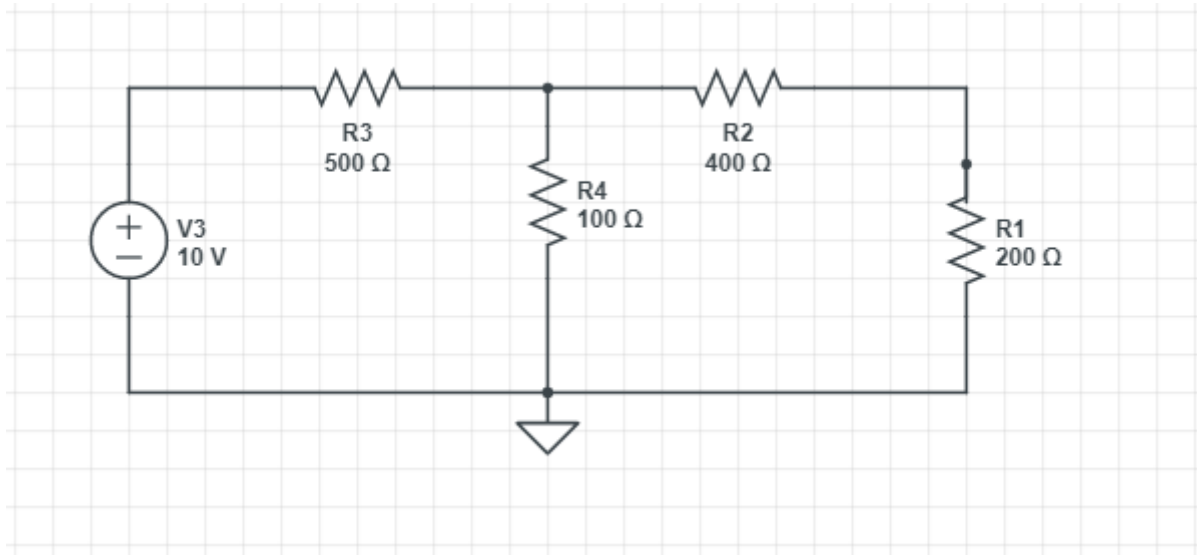2) Draw the circuit below and simulate the Voutput on R1. (use <https://lushprojects.com/circuitjs/circuitjs.html>)



3) Draw and the simulate Half wave rectifier. (<https://lushprojects.com/circuitjs/circuitjs.html>)