
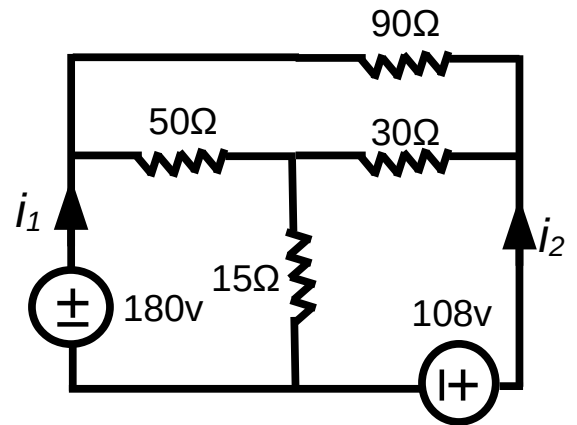


Student Name:

Student No :

Daytime: ☐ Evening: ☐1. (35) Find i_1 and i_2 for the following circuit. (Use which ever method you want)

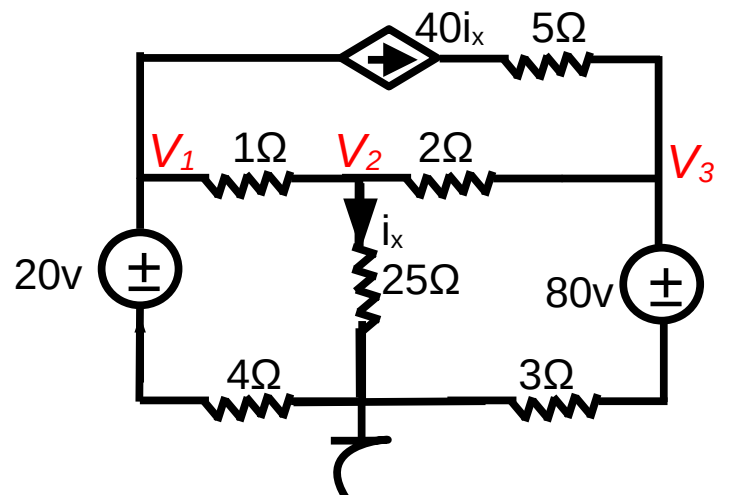2. (35) Write the node-voltage equations and the constraint equation for the following circuit.



3. (35) Write the mesh-current equations and the constraint equation for the following circuit.

