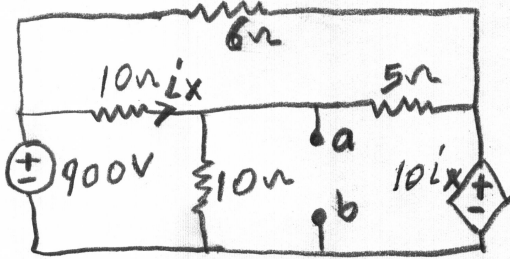
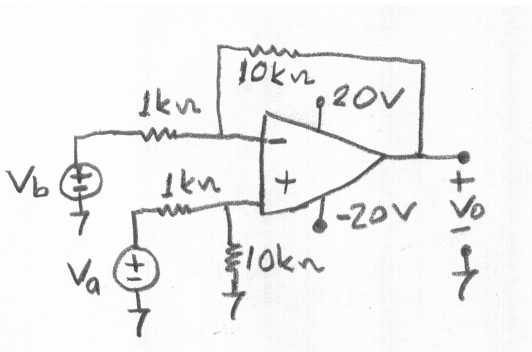


Student Name:

Student No :

Daytime: ☐ Evening: ☐

1. (35) Find the Thevenin equivalent seen from the terminals "a" and "b" of the following circuit.

2. (35) a) Find V_o in terms of V_a and V_b (Assume that the op-amp is ideal and the op-amp works in the linear region)3. (35) Assume $i_g(t) = 8e^{-500t} + 2e^{-1000t}$ Find $V_1(t)$ and the expression for the power delivered to the inductor.